

## 4 Bit Latch Using D Flip Flops

### Latch Definition

A *latch* is an electronic logic circuit that has two inputs and one output. One of the inputs is called the **SET** input; the other is called the **RESET** input.


Latch circuits can be either active-high or active-low. The difference is determined by whether the operation of the latch circuit is triggered by HIGH or LOW signals on the inputs.

- **Active-high circuit:** Both inputs are normally tied to ground (LOW), and the latch is triggered by a momentary HIGH signal on either of the inputs.
- **Active-low circuit:** Both inputs are normally HIGH, and the latch is triggered by a momentary LOW signal on either input.

### More Information:

<http://www.dummies.com/how-to/content/electronics-basics-what-is-a-latch-circuit.html>

### D Flip Flop

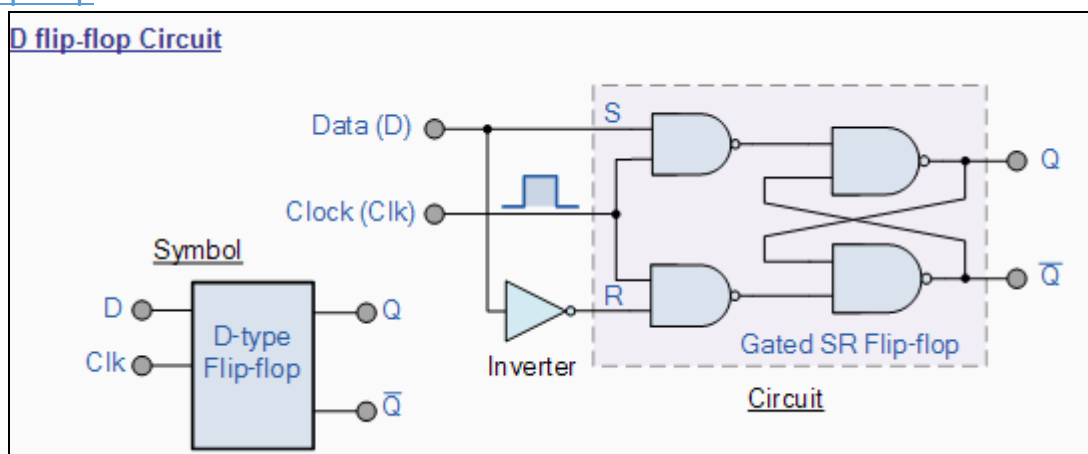


### Truth Table for the D Flip-flop

Clk	D	Q	$\bar{Q}$	Description
$\downarrow \gg 0$	X	Q	$\bar{Q}$	Memory no change
$\uparrow \gg 1$	0	0	1	Reset Q $\gg$ 0
$\uparrow \gg 1$	1	1	0	Set Q $\gg$ 1

Note:  $\downarrow$  and  $\uparrow$  indicates direction of clock pulse as it is assumed D flip-flops are edge triggered

#### 4 Bit Latch Circuit

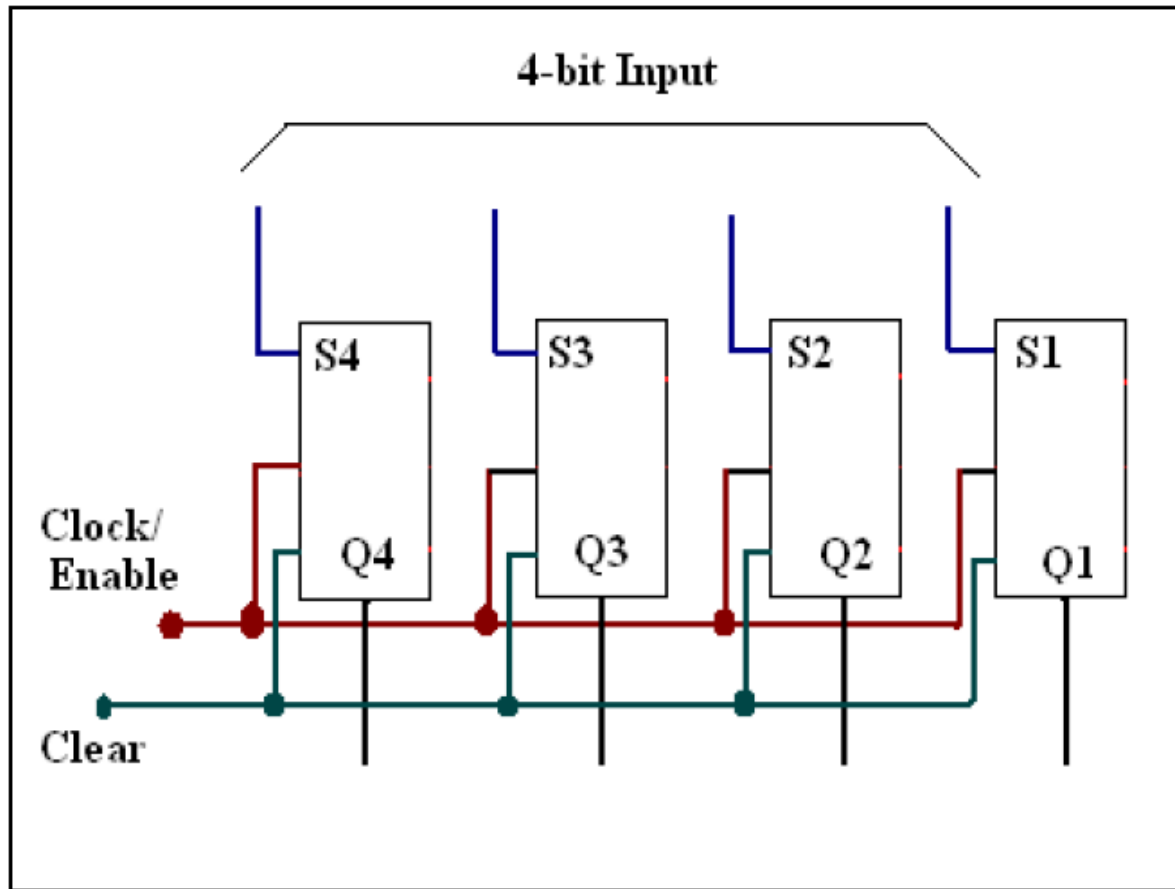

#### 4 Bit Latch Operation

- The clock inputs are connected in parallel.
- The data is placed on the four inputs.
- The data can only pass through to the Q outputs when the clock line goes high (logic 1).
- A clear line allows the latch to be reset.

CLK	D	Q
0	X	last state
1	0	0
1	1	1

CLK → low: D can change without effect on the output

CLK → high: Q is forced to equal the value of D

Ex: Create a 4 bit data memory with D-latches (D-FF).

 


Fig. 7-9: Data storage with D-FF

In Fig. 7-9, when the clock goes high, input data is loaded into the Flip-Flops and appears at the output.

Suppose the data input is:

$$D_3 D_2 D_1 D_0 = 1 0 1 0$$

When the clock goes high this 4 bit word is loaded into the D-latches, resulting in an output of:

$$Q_3 Q_2 Q_1 Q_0 = 1 0 1 0$$